

USN

--	--	--	--	--	--	--	--	--	--

15CS32

Third Semester B.E. Degree Examination, Dec.2018/Jan.2019 Analog and Digital Electronics

Time: 3 hrs.

Max. Marks: 80

Note: Answer FIVE full questions, choosing one full question from each module.

Module-1

- 1 a. Explain the working of N-channel MOSFET, with the help of neat diagram. (08 Marks)
 b. What are applications of FET? (04 Marks)
 c. What are the ideal characteristics of op-amp? (04 Marks)

OR

- 2 a. Explain the performance parameters of op-amp. (08 Marks)
 b. Explain the relaxation oscillator, with the help of neat diagram. (08 Marks)

Module-2

- 3 a. Minimize the following Boolean function using K-map method,
 $F(A, B, C, D) = \sum m(0, 2, 3, 8, 10, 11, 12, 14)$ (06 Marks)
 b. Apply Quine Mc-Cluskey method to find the essential prime implicants for the Boolean expression,
 $F(A, B, C, D) = \sum m(0, 1, 2, 3, 10, 11, 12, 13, 14, 15)$ (10 Marks)

OR

- 4 a. Minimize the following Boolean function using K-map method.
 $F(A, B, C, D) = \prod M(0, 1, 2, 3, 4) + \sum d(5, 7)$ (06 Marks)
 b. What is Hazard? Explain its types with examples. (10 Marks)

Module-3

- 5 a. Implement the following function using 8 : 1 multiplexer
 $F(A, B, C, D) = \sum m(1, 2, 5, 7, 8, 10, 11, 13, 14, 15)$ (06 Marks)
 b. Realize the following function using 3 : 8 decoder
 (i) $F(A, B, C) = \sum m(1, 3, 4)$
 (ii) $F(A, B, C) = \sum m(3, 5, 7)$ (04 Marks)
 c. Design a priority encoder using the truth table. The order of priority for three inputs is $X_1 > X_2 > X_3$ (06 Marks)

Truth Table

Input				Output	
S	X ₁	X ₂	X ₃	A	B
0	X	X	X	0	0
1	1	X	X	0	1
1	0	1	X	1	0
1	0	0	1	1	1
1	0	0	0	0	0

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

OR

- 6 a. Design seven segment decoder using PLA. (08 Marks)
b. Design Half adder and Full adder. (08 Marks)

Module-4

- 7 a. Explain Smith contact bounce circuit. (08 Marks)
b. Give state transition diagram and characteristic equations for SR-FF and JK-FF. (08 Marks)

OR

- 8 a. With neat diagram, explain Ring and Johnson counter. (08 Marks)
b. What is shift register? With neat diagram, explain 4-bit parallel in serial out shift registers. (08 Marks)

Module-5

- 9 a. Define counter. Design mod-8 up synchronous counter using JK-FF. (12 Marks)
b. Write VHDL code for mod-8 up counter. (04 Marks)

OR

- 10 a. Explain the binary ladder with digital of 1000. (06 Marks)
b. Explain with neat diagram, single slope A/D converters. (10 Marks)

* * * * *